
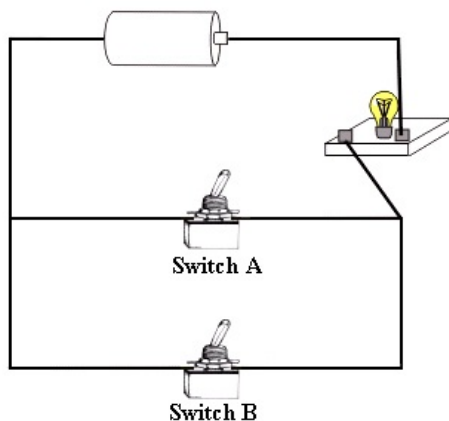


Switching on the bulbs

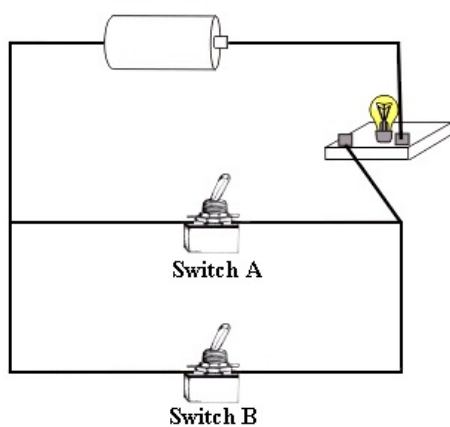This task is about switches in a simple electric circuit.




Look at the electric circuit that has been set up above.



a) If Switch A and Switch B are both turned off, the bulb will be ...

glowing


not glowing

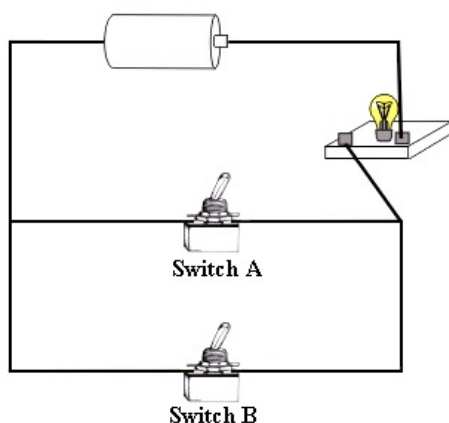

b) If Switch A is turned on and Switch B is turned off, the bulb will be ...

glowing


not glowing

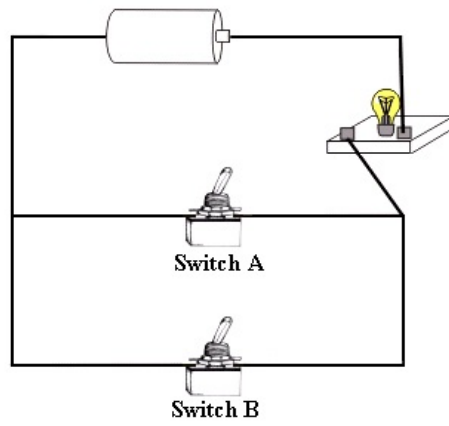

c) If Switch A is turned off and Switch B is turned on, the bulb will be ...

glowing

not glowing

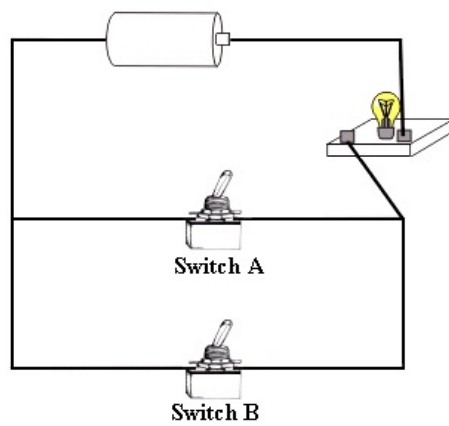

d) If both switches are turned on, the bulb will be ...

glowing

not glowing