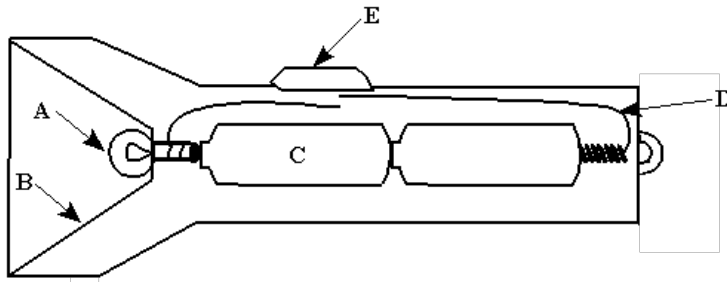


Parts of a torch

This task is about reading information from a diagram.



Match the parts (A, B, C, D, and E) of the torch with the correct name.

a) Draw a line between the part and the name.

Part

A
B
C
D
E

Name

- Battery
- Fuse
- Switch
- Reflective shiny material
- Wire
- Bulb

b) Is the torch in the picture on or off? _____

Explain why you think the torch is on or off.

c) _____

d) Write **two** things that you could do or change to make the light from this torch brighter.

1. _____

2. _____