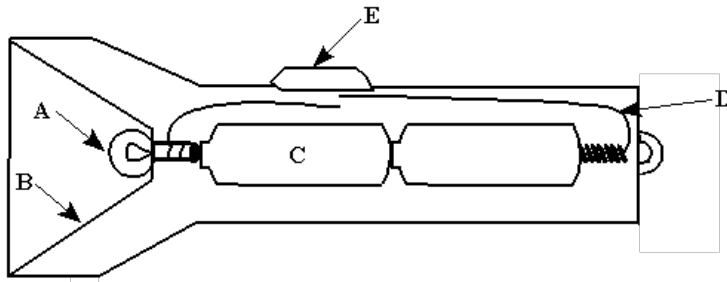


# Parts of a torch

This task is about reading information from a diagram.



Match the parts (A, B, C, D, and E) of the torch with the correct name.

a) Draw a line between the part and the name.

**Part**

**A**  
**B**  
**C**  
**D**  
**E**

**Name**

- Battery
- Fuse
- Switch
- Reflective shiny material
- Wire
- Bulb

b) Is the torch in the picture on or off? \_\_\_\_\_

Explain why you think the torch is on or off.

c) \_\_\_\_\_  
\_\_\_\_\_

d) Write **two** things that you could do or change to make the light from this torch brighter.

1. \_\_\_\_\_
2. \_\_\_\_\_