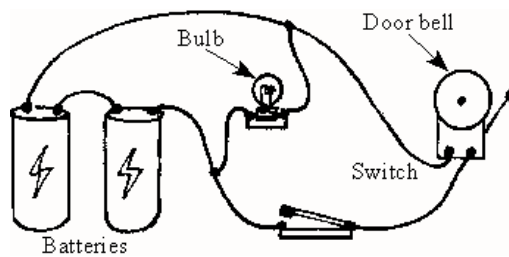


Lights and bells

This task is about reading a circuit diagram.



What happens when the switch is open, as in the diagram?

- ☐ The bulb is lit, but the bell does not ring.
- ☐ The bulb is not lit and the bell does not ring
- ☐ The bulb is lit and the bell rings.
- ☐ The bell rings, but the bulb is not lit.
- ☐ No current flows from the batteries.

Explain your answer.

Published on *Assessment Resource Banks* (<https://arbs.nzcer.org.nz>)