
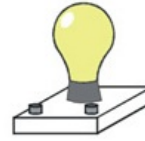


# Add the wires

---

This task is about completing an electric circuit.

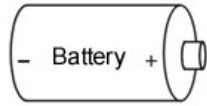a) Draw in wires from the battery to the bulb so that the lights will glow.



b) Draw in wires from the battery to the bulbs so that the lights will glow.

