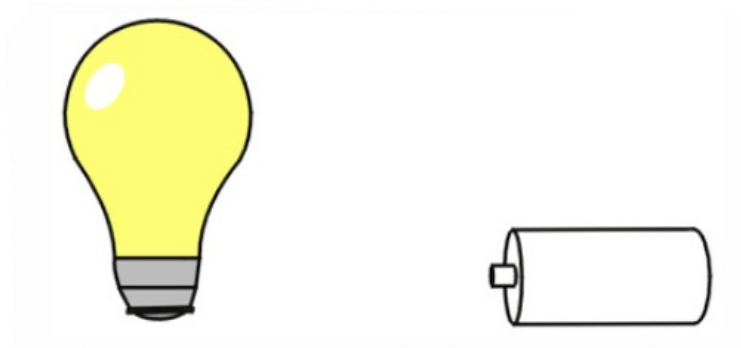


Light up the bulb

This task is about electric circuits.

On the diagram, draw the two wires that are needed to be between the battery and the bulb to make the bulb shine.



Published on <https://newzealandcurriculum.tahurangi.education.govt.nz>