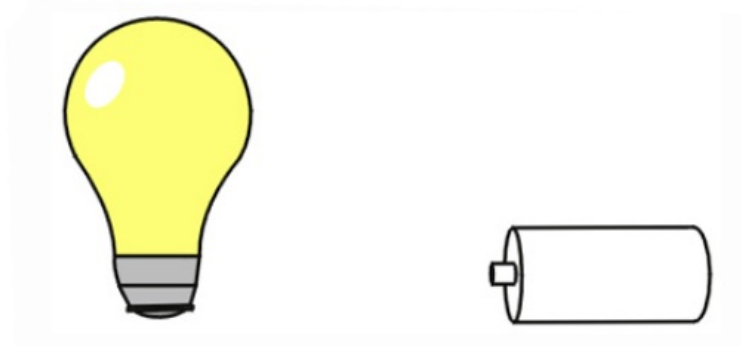


# Light up the bulb

---

**This task is about electric circuits.**

On the diagram, draw the two wires that are needed to be between the battery and the bulb to make the bulb shine.



Published on *Assessment Resource Banks* (<https://arbs.nzcer.org.nz>)