

Drawing circuit diagrams

a) Draw a line to match each symbol with its correct name. One name is not needed.

Symbol

Name



• fuse



• bell



• cell



• lamp




• wire

• closed switch



• battery

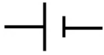

• open switch

b) Use the symbols to draw a circuit which has a:

- battery
- bell and a lamp in series
- switch that is open

Circuit Drawing