

Drawing circuit diagrams

a) Draw a line to match each symbol with its correct name. One name is not needed.

Symbol

Name



- fuse



- bell



- cell



- lamp




- wire

- closed switch



- battery

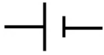

- open switch

b) Use the symbols to draw a circuit which has a:

- battery
- bell and a lamp in series
- switch that is open

Circuit Drawing