

# Drawing circuit diagrams

a) Draw a line to match each symbol with its correct name. One name is not needed.

**Symbol**

**Name**



• fuse



• bell



• cell




• lamp



• wire



• closed switch

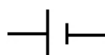

• battery

• open switch

b) Use the symbols to draw a circuit which has a:

- battery
- bell and a lamp in series
- switch that is open

Circuit Drawing