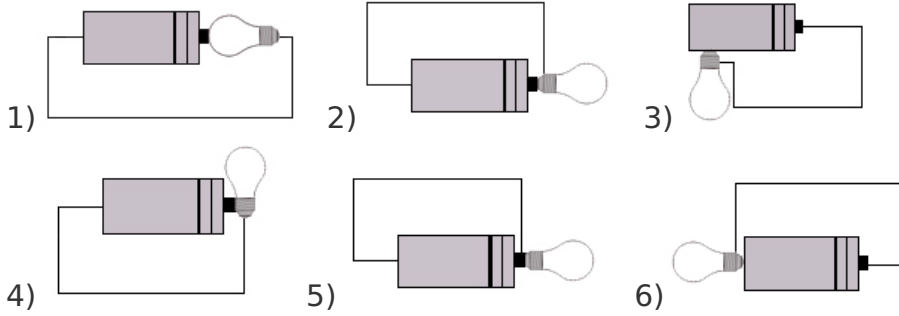


Circuit investigations


What is a circuit?

a) i) Using the equipment you have, test each of the following circuits. Put a tick over it if it works, or a cross if it doesn't.



ii) Why do some of the circuits work, while others do not?

b) Now make up these two circuits.

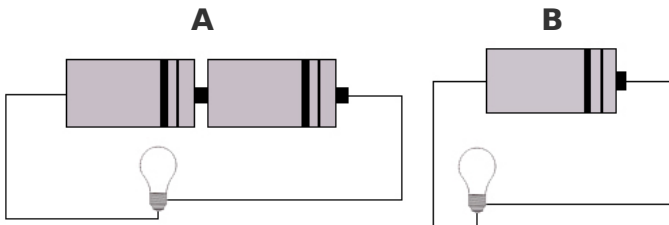

i) What did you find out?

ii) Explain why this happened.

c) Make up these two circuits and explain your results.

