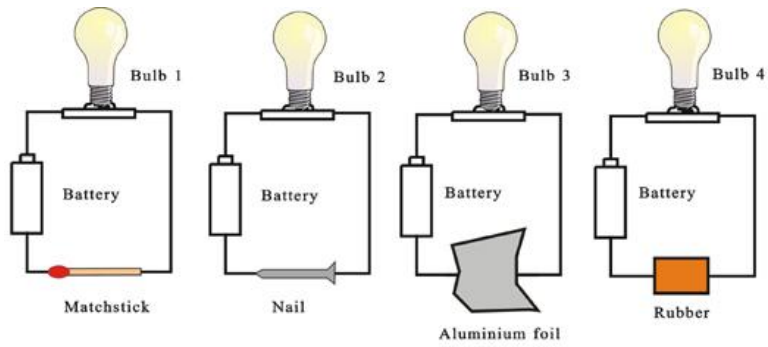


# Electricity conductors

This task is about how some materials can conduct electricity.



Using the information in the diagrams above, which of the bulbs will light up?

- 1 and 2
- 2 and 3
- 3 and 4
- 1, 2, and 3
- 2, 3, and 4

Why would the bulbs you chose light up?