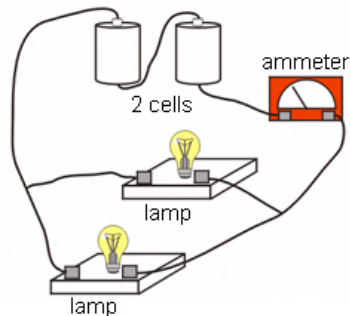
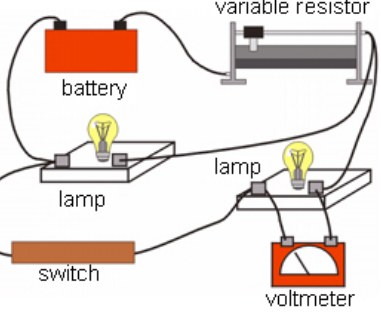


# Circuit diagrams II

This task is about drawing electric circuit diagrams.

Draw a standard circuit diagram for each circuit shown below.

<p>a)</p>  <p>2 cells</p> <p>ammeter</p> <p>lamp</p> <p>lamp</p>	<p>Circuit Diagram</p>
<p>b)</p>  <p>battery</p> <p>variable resistor</p> <p>lamp</p> <p>lamp</p> <p>switch</p> <p>voltmeter</p>	<p>Circuit Diagram</p>