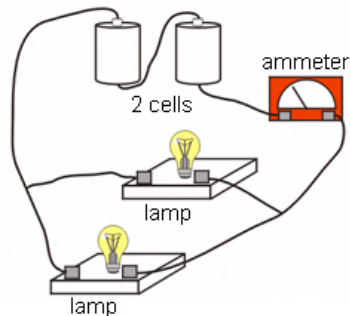
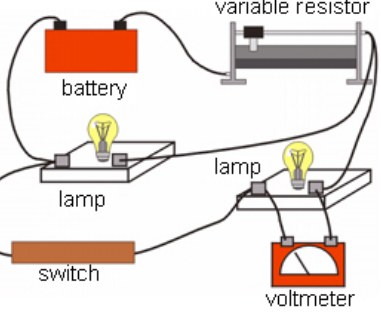


# Circuit diagrams II

This task is about drawing electric circuit diagrams.

Draw a standard circuit diagram for each circuit shown below.

<p>a)</p>  <p>2 cells ammeter lamp lamp</p>	<p>Circuit Diagram</p>
<p>b)</p>  <p>battery variable resistor lamp lamp switch voltmeter</p>	<p>Circuit Diagram</p>