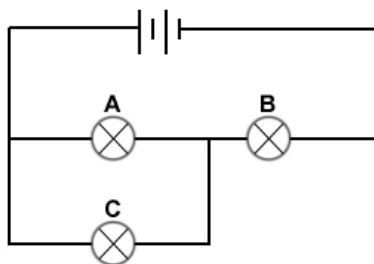


# Parallel and series

---



Use the circuit above to answer the following questions.

a) Which bulbs are in parallel? \_\_\_\_\_

b) Which bulbs are in series? \_\_\_\_\_

c) If all the bulbs have the same resistance, which bulbs would have the same current flowing through them?

\_\_\_\_\_

d) Draw a switch in the circuit above so that bulb A can be turned off when bulb C and bulb B are still going.

Published on *Assessment Resource Banks* (<https://arbs.nzcer.org.nz>)